

# Processor Design

Spencer Melnick

December 19, 2018

## Contents

<b>1</b>	<b>Introduction</b>	<b>2</b>
<b>2</b>	<b>Modules</b>	<b>2</b>
2.1	Adder . . . . .	2
2.1.1	Half Adder . . . . .	2
2.1.2	Full Adder . . . . .	4
2.1.3	2 Bit Adder . . . . .	6
2.1.4	4 Bit Adder . . . . .	8
2.1.5	8 Bit Adder . . . . .	9
2.1.6	16 Bit Adder . . . . .	10
2.1.7	32 Bit Adder . . . . .	12
2.2	32 Bit Multiplier . . . . .	14
2.3	32 Bit Divider . . . . .	16
2.4	32 Bit ALU . . . . .	19

# **1 Introduction**

## **2 Modules**

### **2.1 Adder**

The adder used in this processor is a simple 32 bit ripple-carry adder. The 32 bit adder is created using a series of smaller adder modules including:

- Half Adder
- Full Adder
- 2 Bit Adder
- 4 Bit Adder
- 16 Bit Adder
- 32 Bit Adder

#### **2.1.1 Half Adder**

##### **2.1.1.1 Inputs**

- Operand A - 1 bit
- Operand B - 1 bit

##### **2.1.1.2 Outputs**

- Sum - 1 bit
- Carry - 1 bit

##### **2.1.1.3 Functionality**

Takes two single bit operands and produces the single bit sum and the carry bit.

##### **2.1.1.4 Diagrams**

 


Figure 1: Logic diagram of the half adder

#### 2.1.1.5 Testing

All possible inputs for the half adder are stimulated by the test bench and are compared to the expected outputs according to the following table:

A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1



Figure 2: Simulation output of half adder

## 2.1.2 Full Adder

### 2.1.2.1 Inputs

- Operand A - 1 bit
- Operand B - 1 bit
- Carry In - 1 bit

### 2.1.2.2 Outputs

- Sum - 1 bit
- Carry Out - 1 bit

### 2.1.2.3 Functionality

Takes three single bit operands and produces the single bit sum and the carry bit.

### 2.1.2.4 Diagrams

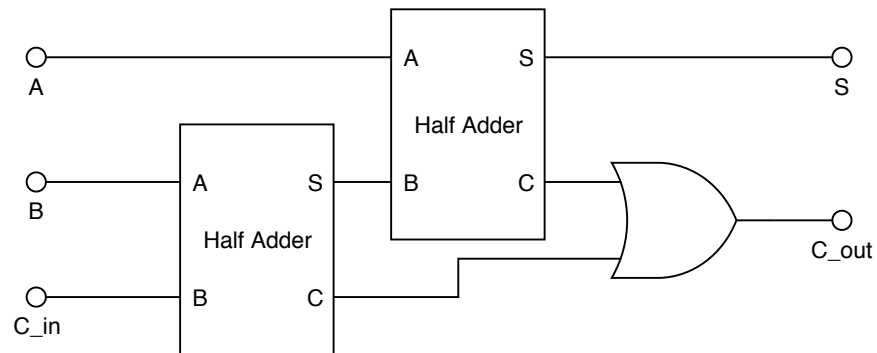


Figure 3: Logic diagram of the full adder

### 2.1.2.5 Testing

All possible inputs for the full adder are stimulated by the test bench and are compared to the expected outputs according to the following table:

A	B	Carry In	S	Carry Out
0	0	0	0	0
1	0	0	1	0
0	1	0	1	0
1	1	0	0	1
0	0	1	1	0
1	0	1	0	1
0	1	1	0	1
1	1	1	1	1



Figure 4: Simulation output of full adder

### 2.1.3 2 Bit Adder

#### 2.1.3.1 Inputs

- Operand A - 2 bit
- Operand B - 2 bit
- Carry In - 1 bit

#### 2.1.3.2 Outputs

- Sum - 2 bit
- Carry Out - 1 bit

### 2.1.3.3 Functionality

Takes two 2 bit operands and a third single bit operand and produces the 2 bit sum and the carry bit.

### 2.1.3.4 Diagrams

 


Figure 5: Logic diagram of the 2 bit adder

### 2.1.3.5 Testing

Due to the larger range of possible inputs, inputs are selected to include several base cases, as well as the maximum input value case and minimum input value case. The inputs and expected outputs are as follows:

A	B	Carry In	S	Carry Out
3	3	0	2	1
3	1	0	0	1
3	3	1	3	1
0	0	0	0	0

 


Figure 6: Simulation output of 2 bit adder

## 2.1.4 4 Bit Adder

### 2.1.4.1 Inputs

- Operand A - 4 bit
- Operand B - 4 bit
- Carry In - 1 bit

### 2.1.4.2 Outputs

- Sum - 4 bit
- Carry Out - 4 bit



### 2.1.4.3 Functionality

Takes two 4 bit operands and a third single bit operand and produces the 4 bit sum and the carry bit.

### 2.1.4.4 Diagrams

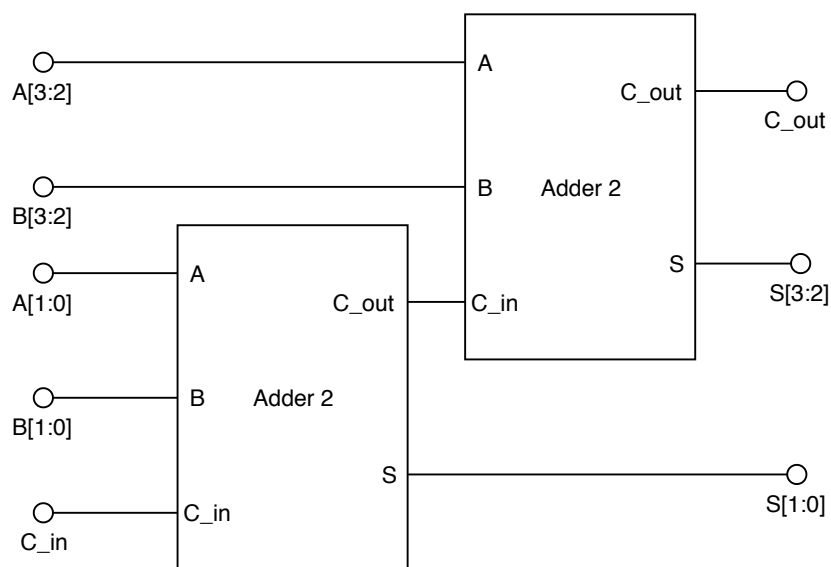


Figure 7: Logic diagram of the 4 bit adder

### 2.1.4.5 Testing

As this module follows a nearly identical functionality as the 2 bit adder, and nearly identical Verilog code, testing was ommitted. This module's test is included within the 32 bit adder test, as the 32 bit adder will only function correctly if this module functions correctly.

## 2.1.5 8 Bit Adder

### 2.1.5.1 Inputs

- Operand A - 8 bit
- Operand B - 8 bit
- Carry In - 1 bit

### 2.1.5.2 Outputs

- Sum - 8 bit
- Carry Out - 8 bit

### 2.1.5.3 Functionality

Takes two 8 bit operands and a third single bit operand and produces the 8 bit sum and the carry bit.

### 2.1.5.4 Diagrams

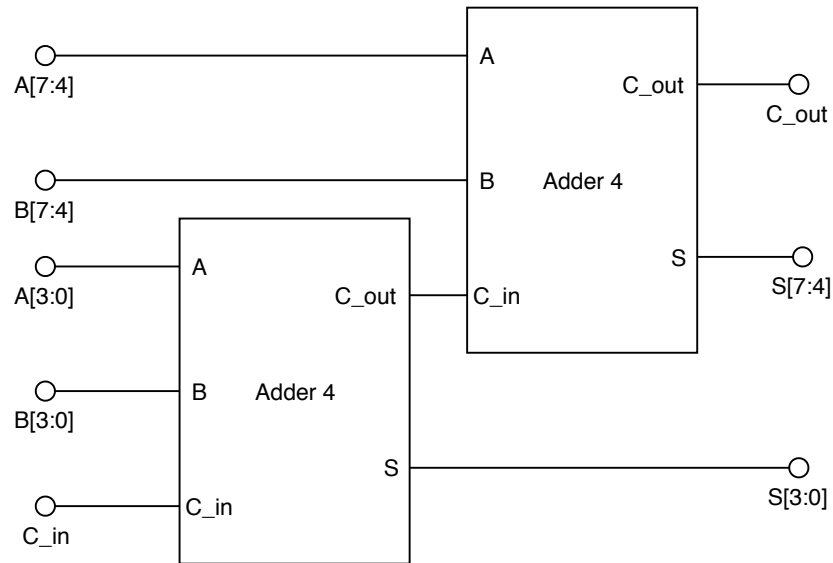


Figure 8: Logic diagram of the 8 bit adder

### 2.1.5.5 Testing

As this module follows a nearly identical functionality as the 2 bit adder, and nearly identical Verilog code, testing was ommitted. This module's test is included within the 32 bit adder test, as the 32 bit adder will only function correctly if this module functions correctly.

## 2.1.6 16 Bit Adder

### 2.1.6.1 Inputs

- Operand A - 16 bit
- Operand B - 16 bit
- Carry In - 1 bit

#### 2.1.6.2 Outputs

- Sum - 16 bit
- Carry Out - 16 bit

#### 2.1.6.3 Functionality

Takes two 16 bit operands and a third single bit operand and produces the 16 bit sum and the carry bit.

#### 2.1.6.4 Diagrams

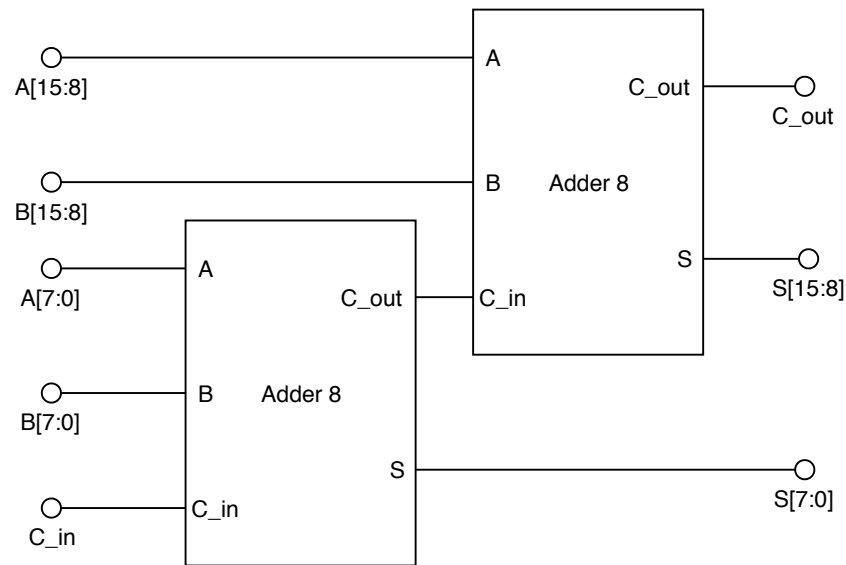


Figure 9: Logic diagram of the 16 bit adder

#### 2.1.6.5 Testing

As this module follows a nearly identical functionality as the 2 bit adder, and nearly identical Verilog code, testing was ommitted. This module's test is included within the 32 bit adder test, as the 32 bit adder will only function correctly if this module functions correctly.

## 2.1.7 32 Bit Adder

### 2.1.7.1 Inputs

- Operand A - 32 bit
- Operand B - 32 bit
- Carry In - 1 bit

### 2.1.7.2 Outputs

- Sum - 32 bit
- Carry Out - 32 bit

### 2.1.7.3 Functionality

Takes two 32 bit operands and a third single bit operand and produces the 32 bit sum and the carry bit.

### 2.1.7.4 Diagrams

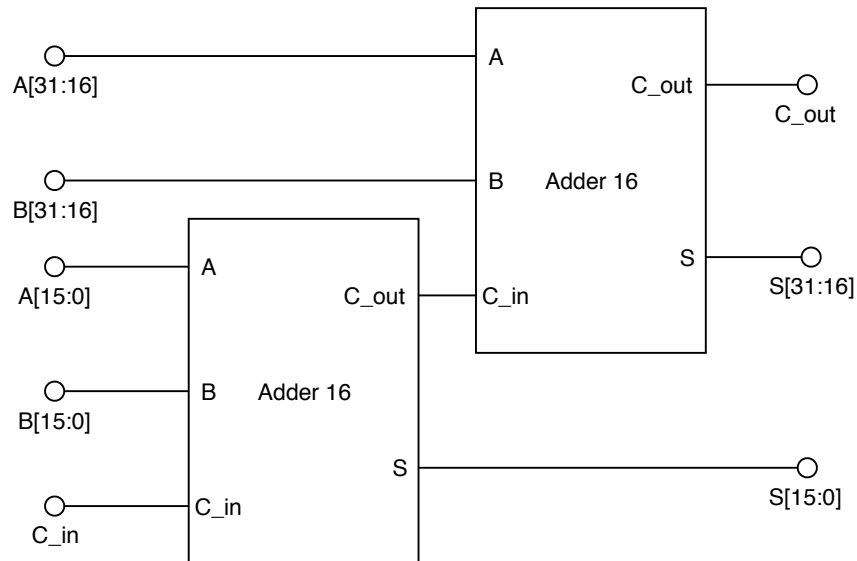


Figure 10: Logic diagram of the 32 bit adder

### 2.1.7.5 Testing

Due to the larger range of possible inputs, inputs are selected to include several base cases, as well as the maximum input value case. The inputs and expected outputs are as follows:

A	B	Carry In	S	Carry Out
10	10	1	21	0
1	0	1	2	0
4294967295	0	1	0	1
4294967295	4294967295	1	4294967295	1

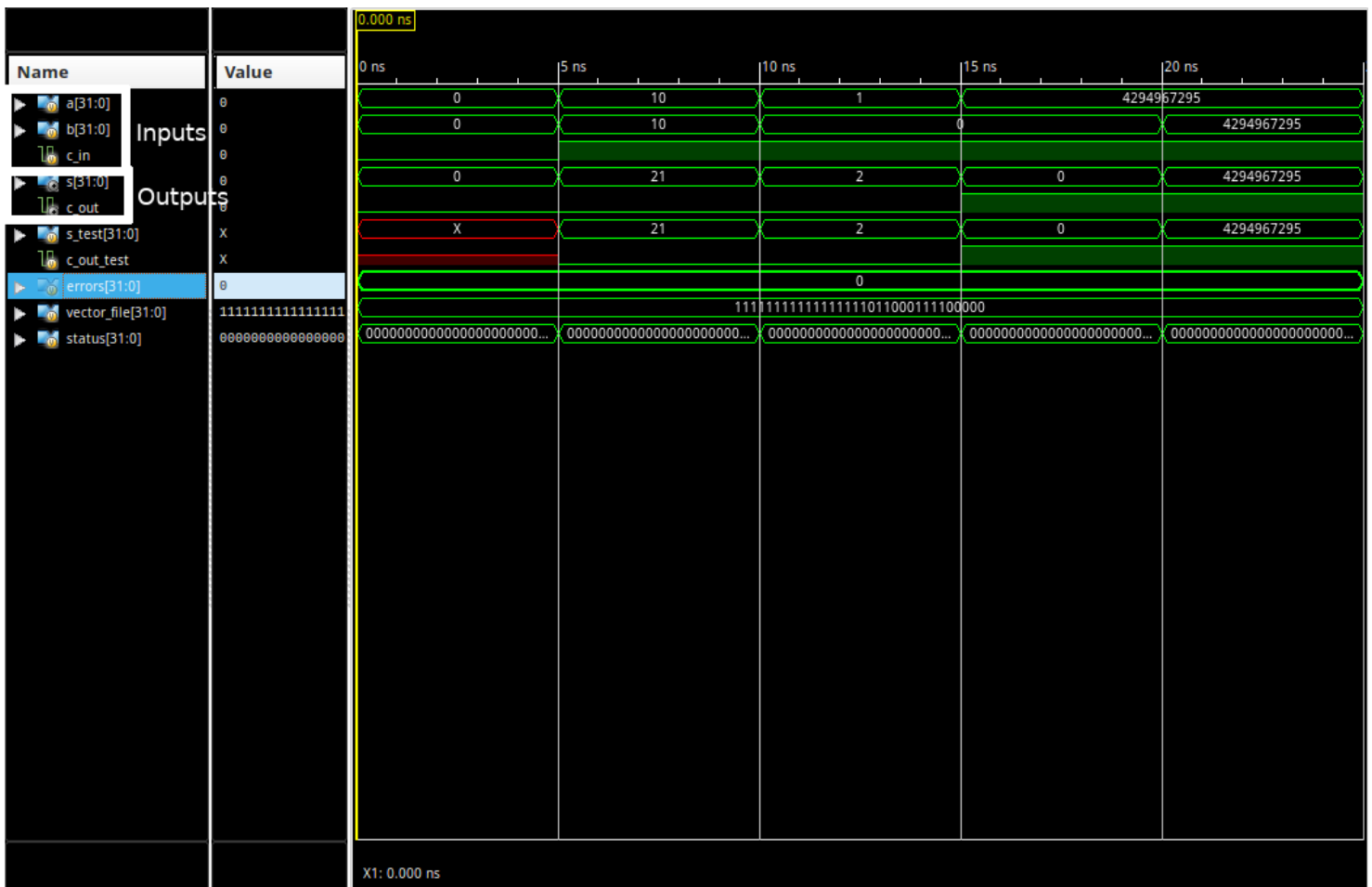


Figure 11: Simulation output of 32 bit adder

## **2.2 32 Bit Multiplier**

### **2.2.0.1 Inputs**

- Operand A - 32 bit
- Operand B - 32 bit
- Clock Signal - 1 bit
- Enable Signal - 1 bit
- Reset Signal - 1 bit

### **2.2.0.2 Outputs**

- Product - 64 bit
- Done Signal - 1 bit

### **2.2.0.3 Functionality**

The multiplier module uses a simple multiplication algorithm, optimized to use the minimum number of gates. As a consequence, the multiplier module takes multiple clock cycles to complete an operation.

On the positive edge of the reset signal, the values of operand A and operand B are stored by the multiplier and the multiplication is reset, but no actual multiplication is performed.

If the enable signal is high, then on the positive edge of the clock signal the module will complete one cycle of the multiplication operation. During this time the product output will change, but it will not be the correct value.

Once the multiplication is complete, the output done signal will be driven high and the product will be accurate.

This module supports signed multiplication.

### **2.2.0.4 Diagrams**

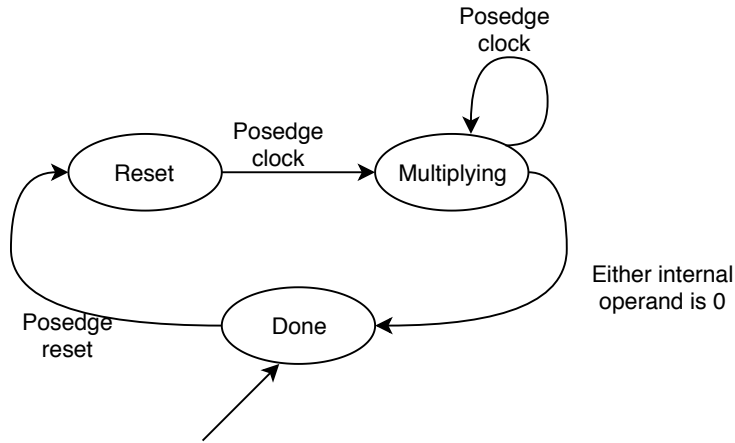


Figure 12: State change diagram of the 32 bit multiplier

#### 2.2.0.5 Testing

A few base cases are tested with positive and negative number multiplication, multiplication by zero, and the largest positive inputs and largest negative inputs are tested. Overflow is not tested, as with a 64 bit product, overflow is impossible. The inputs and expected outputs are as follows:

A	B	Product
5	10	50
7	5	35
0	0	0
1	0	0
1	1	1
1	-1	-1
-1	-1	1
2147483647	2147483647	4611686014132420609
-2147483648	-2147483648	4611686018427387904

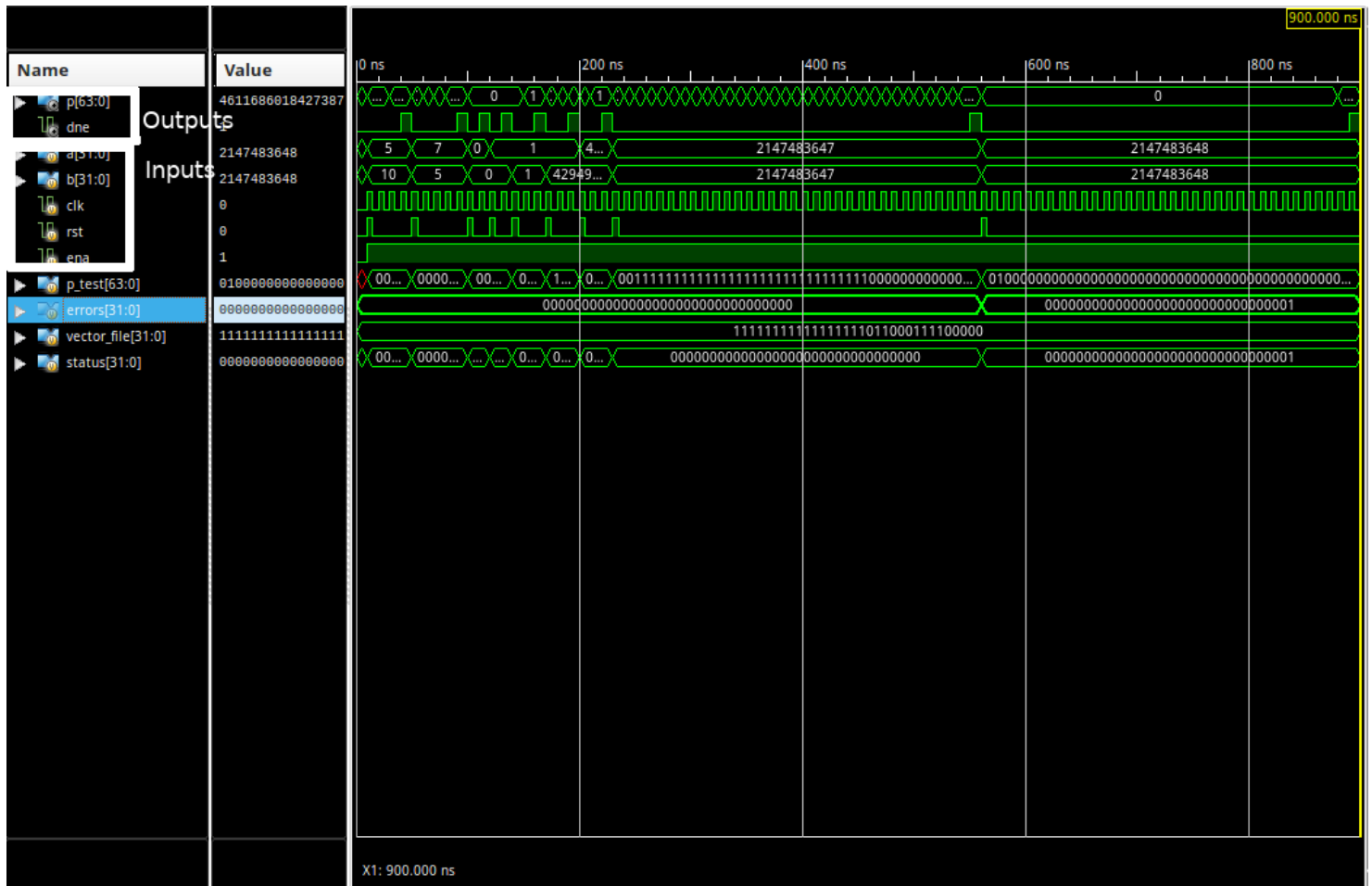


Figure 13: Simulation output of 32 bit multiplier

## 2.3 32 Bit Divider

### 2.3.0.1 Inputs

- Dividend - 32 bit
- Divisor - 32 bit
- Clock Signal - 1 bit
- Enable Signal - 1 bit
- Reset Signal - 1 bit



### 2.3.0.2 Outputs

- Quotient - 32 bit
- Remainder - 32 bit
- Done Signal - 1 bit

### 2.3.0.3 Functionality

The multiplier module uses a simple division algorithm, optimized to use the minimum number of gates. As a consequence, the division module takes multiple clock cycles to complete an operation.

On the positive edge of the reset signal, the values of the dividend and divisor are stored by the multiplier and the division is reset, but no actual division is performed.

If the enable signal is high, then on the positive edge of the clock signal the module will complete one cycle of the division operation. During this time the quotient output and remainder outputs will change, but it will not be the correct value.

Once the division is complete, the output done signal will be driven high and the quotient and remainder will be accurate.

This module supports signed division.

### 2.3.0.4 Diagrams

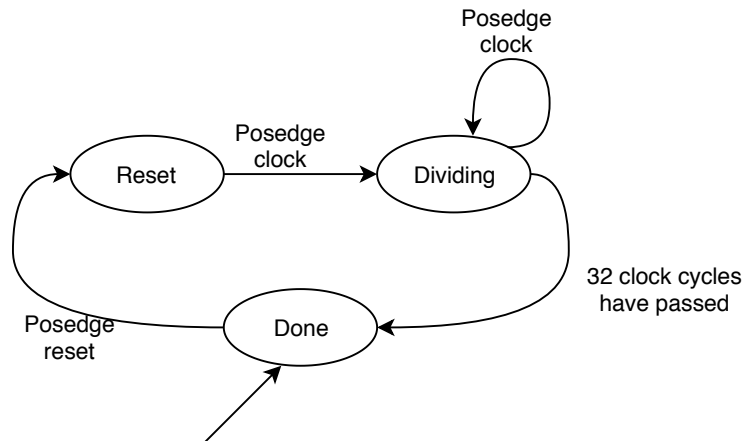


Figure 14: State change diagram of the 32 bit multiplier

### 2.3.0.5 Testing

A few base cases are tested with positive and negative number division inputs and largest negative inputs are tested. Division by 0 is not handled. The inputs and expected outputs are as follows:

A	B	Quotient	Remainder
100	25	4	0
175	100	1	75
10	10000	0	10
0	1	0	0
1	1	1	0
-1	1	-1	0
-1	-1	1	0

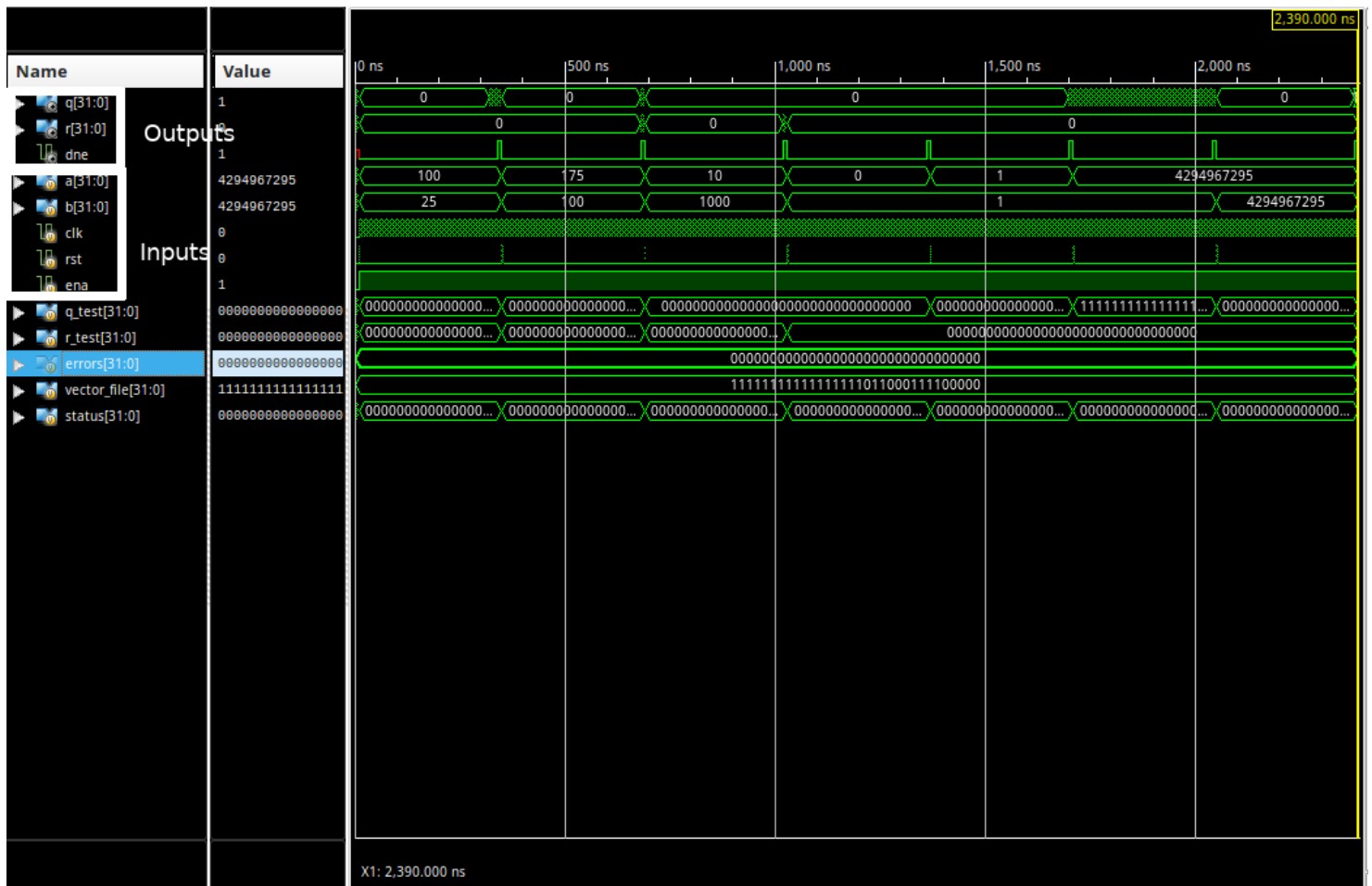


Figure 15: Simulation output of 32 bit multiplier

## 2.4 32 Bit ALU

### 2.4.0.1 Inputs

- Operand A - 32 bit
- Operand B - 32 bit
- Operation - 3 bit
- Clock Signal - 1 bit
- Enable Signal - 1 bit
- Reset Signal - 1 bit

### 2.4.0.2 Outputs

- Result - 32 bit
- Extra - 32 bit
- Done Signal - 1 bit

### 2.4.0.3 Functionality

The 32 bit ALU utilizes the 32 bit adder, multiplier, and divider modules described above. A multiplexer is used to select the appropriate output from the module, depending on the operation code used.

As this module implements a multiplier and divider that take several clock cycles to complete, this ALU requires a reset and clock signal. On the positive edge of the reset signal the values of the operands are stored and the reset for the arithmetic submodule is triggered.

Because a multiplexer is used, the operation code must remain constant throughout the duration of the operation. Like the multiplier and divider, a done signal is driven high on the completion of any operation.

The lower 32 bits of the operation result are stored in the result output, while any additional operation results are stored in the extra output. This includes the carry/borrow bit from the addition/subtraction operation, the upper 32 bits of the product, or the 32 bits of the remainder.

The subtraction operation is implemented by taking the inverse of the second operand and driving the adder's carry in high.

The different codes for operations are as follows:

Operation	Code
Add	0
Subtract	1
Multiply	2
Divide	3

### 2.4.0.4 Diagrams

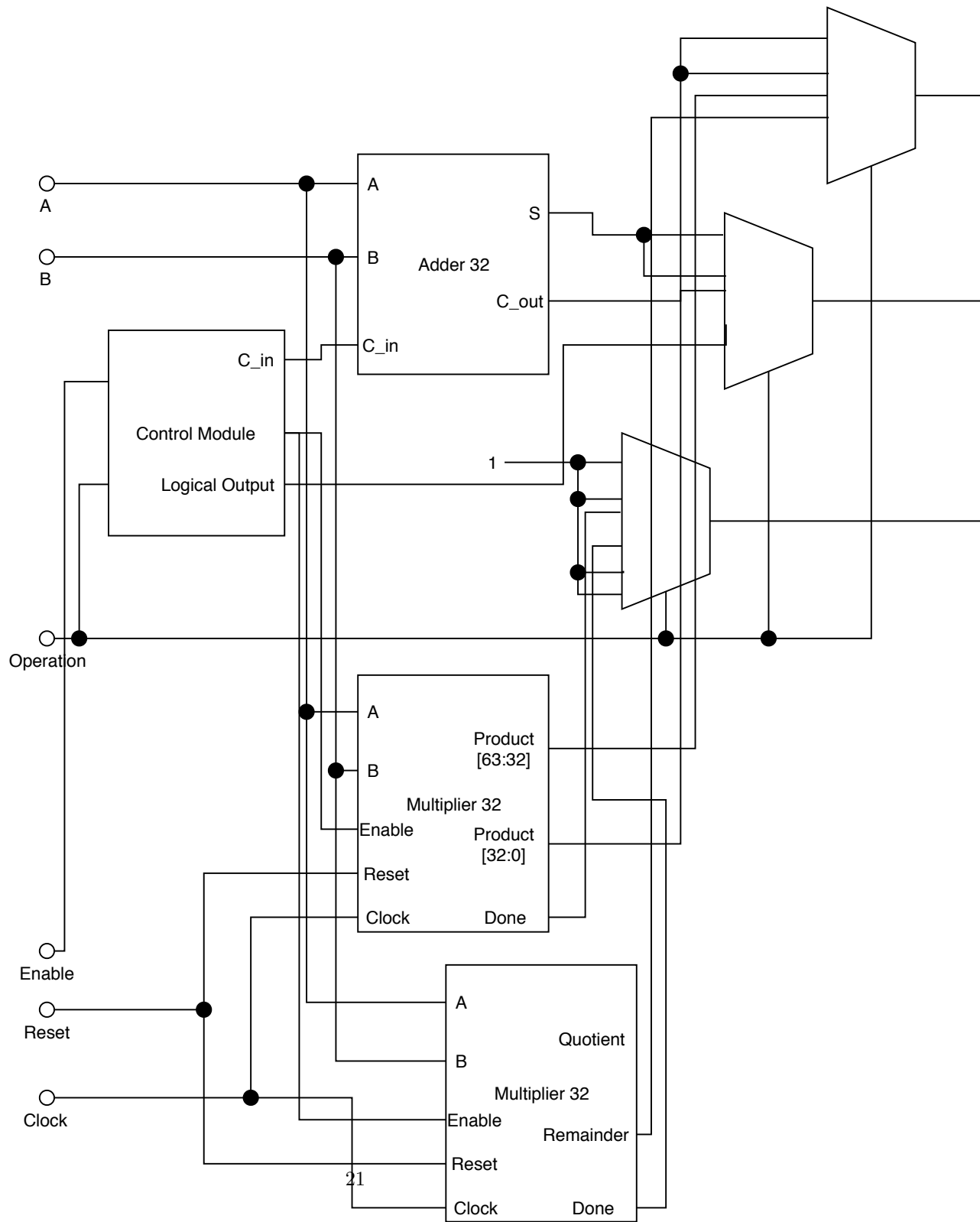


Figure 16: Logical diagram of the 32 bit ALU

#### 2.4.0.5 Testing

As each submodule has been tested individually, only one of each type of operation is tested. The inputs and expected outputs are as follows:

A	B	Operation	Result	Extra
1	2	0	3	0
3	4	1	-1	0
5	6	2	30	0
7	8	3	0	7



Figure 17: Simulation output of 32 ALU